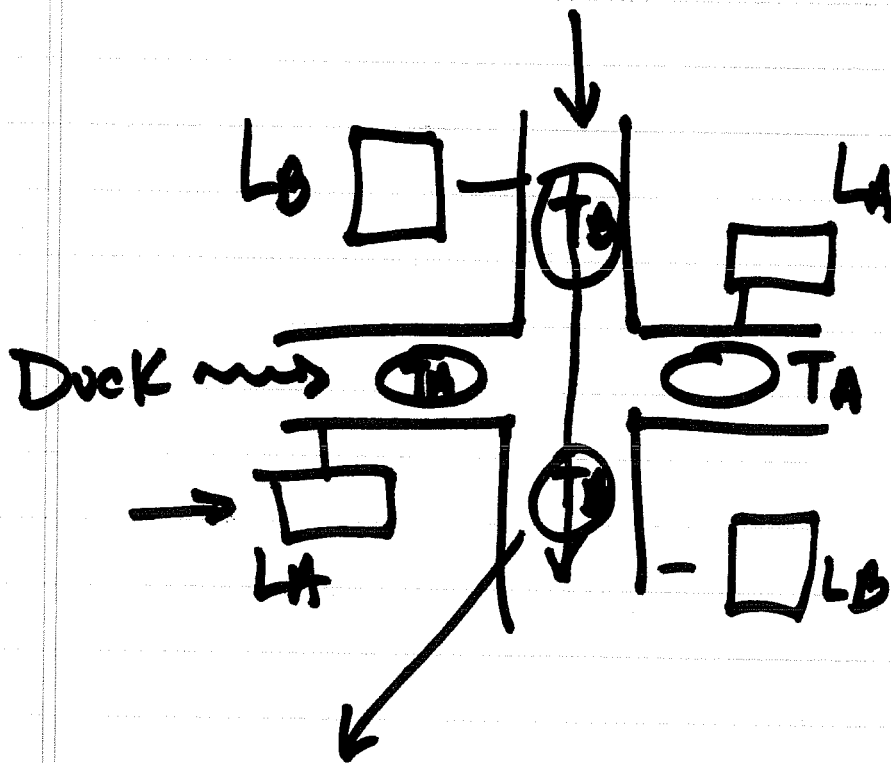


Midterm: 3/3/09

Sequential Circuits: Finite State Machines


McElroy Pipelining



sensor = sense between cars
and no cars

FSM Methodology

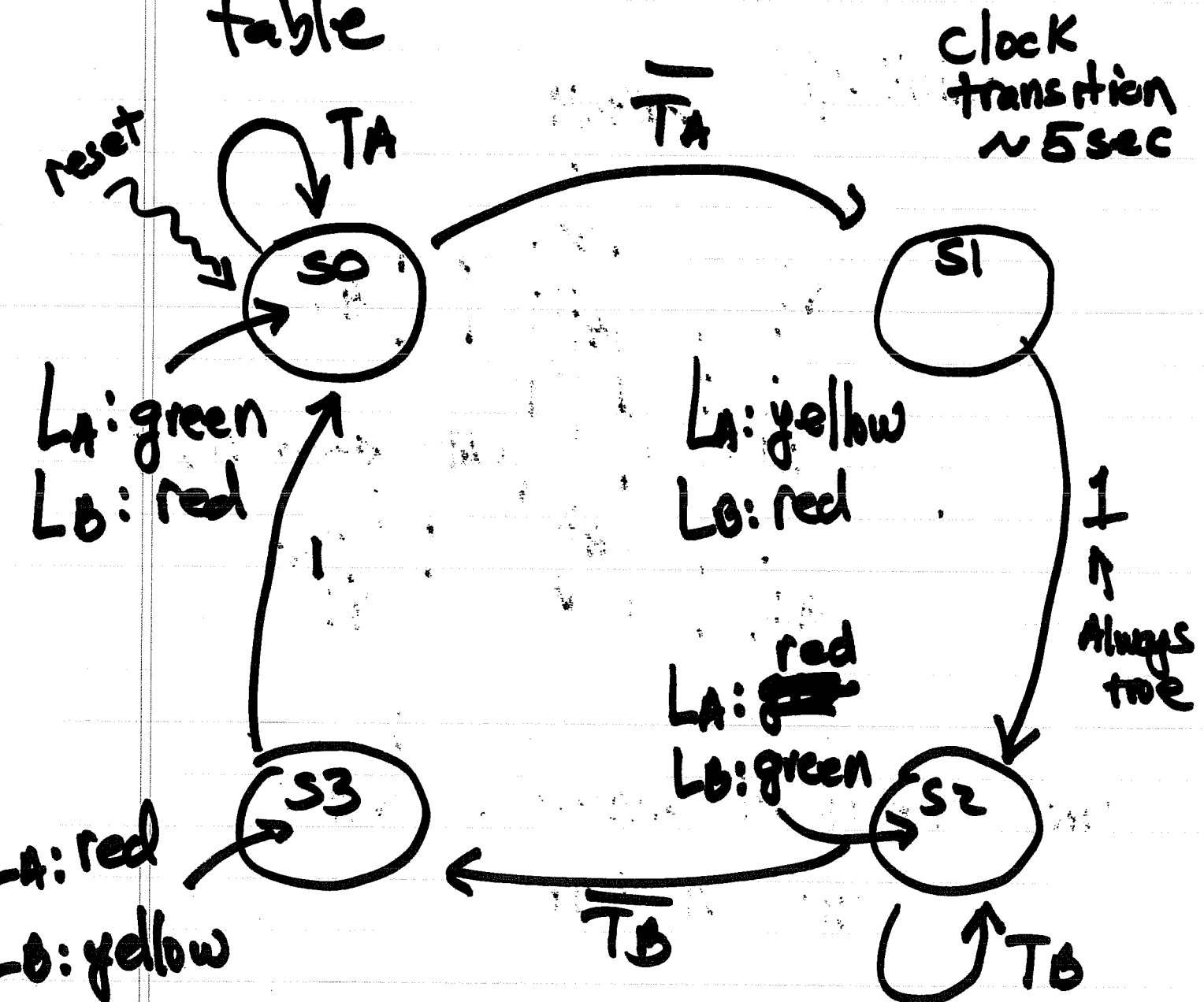1.) Create state diagram and/or state transition table



State Transition TABLE

Current State	Inputs		Next State	Outputs	
	T _A	T _B		L _A	L _B
S ϕ	1	X	S ϕ	G	R
S ϕ	ϕ	X	S1	G	R
S1	X	X	S2	Y	R
S2	X	1	S2	R	G
S2	X	ϕ	S3	R	G
S3	X	X	S ϕ	R	Y

encoding $\hat{=}$ mapping from one element to another

osu \longrightarrow Awesome!

N inputs $\longrightarrow 2^N$ outputs

2 inputs

4 outputs

A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Binary encoding one-hot encoding

2) Encode state transition table with all inputs and all outputs

State	Encoding
S0	00
S1	01
S2	10
S3	11

Binary Encoding
 $\# \text{ bits} = \log_2(\# \text{ states})$

Inputs	Encoding	Outputs	Encoding
$\overline{T_A}$	0	R	00
T_A	1	Y	01
		U	10
		X	11

True →

future enhancement →

3.) Map encoding from #2 to the table in step #1

Current State		Inputs		Next State ^{n.s.}		Outputs	
Z_1	Z_0	T_A	T_B	Z_1^*	Z_0^*	L_A	L_B
0	0	1	X	0	0	10	00
0	0	0	X	0	1	10	00
0	1	X	X	1	0	01	00
1	0	X	1	1	0	00	10
1	0	X	0	1	1	00	10
1	1	X	X	0	0	00	01

4.) Simplify table from
 step #3 using a K-map
 or similar process

$Z_1 Z_0$

$T \backslash TB$

	00	01	11	10
00		1		1
01		1		1
11		1		1
10		1		1

$$Z_1^* = \bar{Z}_1 Z_0 + Z_1 \bar{Z}_0$$

$$z_0^* = \overline{z_1} \overline{z_0} \overline{T_A} + z_1 \overline{z_0} \overline{T_B}$$

$$L_{A1} = \overline{z_1}$$

$$L_{A0} = z_1 \cdot z_0$$

$$L_{B1} = z_1$$

$$L_{B0} = \overline{z_1} \cdot z_0$$

5.) Draw the implementation (schematic)