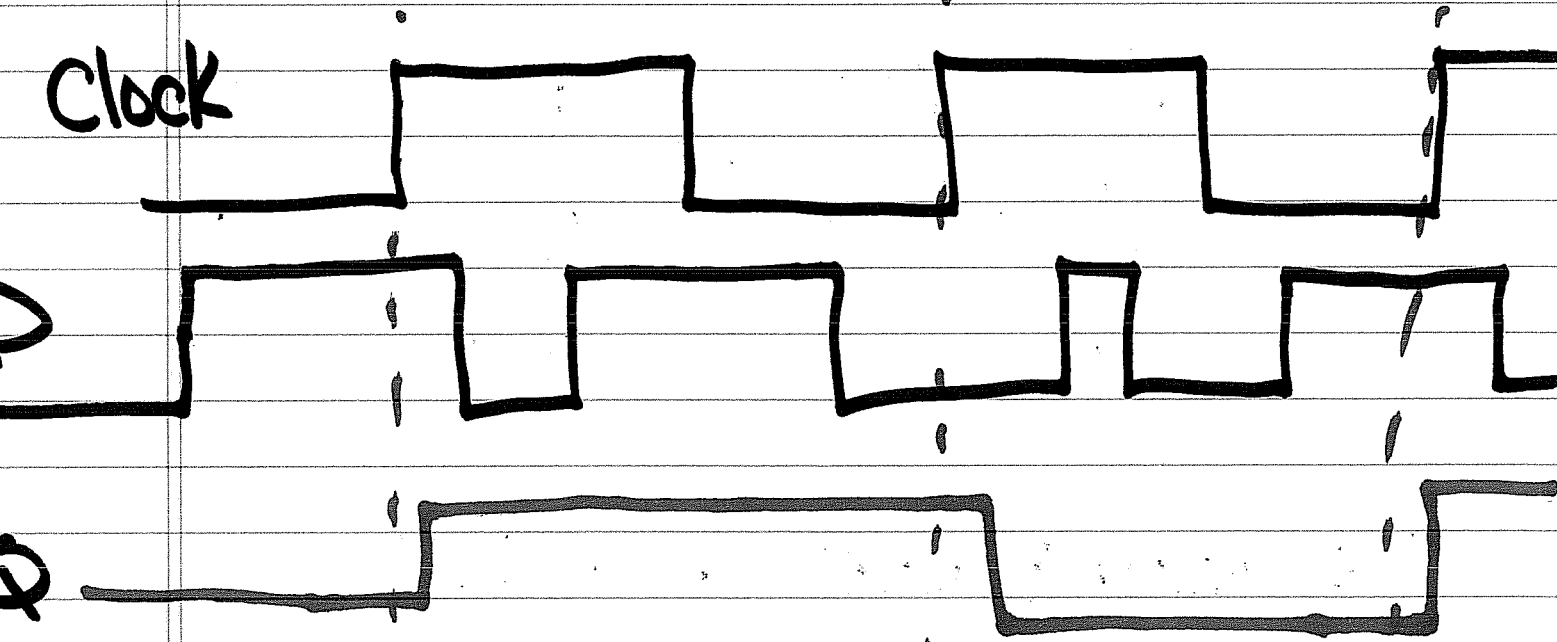


# Quiz

Complete the waveform for a D Flip-Flop



Assuming a positive-edge triggered DFF