

QUIZ

Show a block diagram of a 2-bit Ripple Carry Adder.

$a[1:0]$ $b[1:0]$

Answer.

